

Week 4: - Attenuators

Attenuators:

- Attenuator is a four terminal network, inserted between an input and output.
- It produces a specific amount of loss for current and voltage.

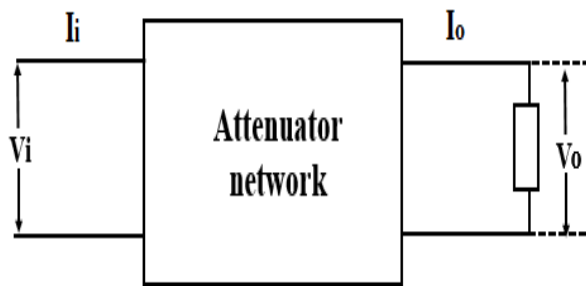


Figure shows the attenuator circuit where,

$V_o \rightarrow$ Output voltage in volts, $V_i \rightarrow$ Input voltage in volts

$I_o \rightarrow$ Output current in amps, $I_i \rightarrow$ Input current in amps

$P_o \rightarrow$ Power output in watts, $P_i \rightarrow$ Power input in watts

Classification of attenuators: Attenuators can be classified as

1. Symmetrical attenuator:

It is resistive network installed between source and load having equal input and output resistance.

Symmetrical attenuator is further classified as:

- i) T type
- ii) Π type

2. Asymmetrical attenuator:

It is resistive network installed between source and load having unequal input and output resistance.

3. Fixed attenuator:

Fixed attenuator provides fixed amount of attenuation. It is also called as pad.

4. Variable attenuator:

Variable attenuator are attenuators whose attenuation can be varied.

Applications of attenuator: Attenuators are used

- In radio communication and transmission line to weaken a stronger signal.
- As volume controls in broadcasting stations
- For matching circuits
- To enhance the input impedance of equipment or instruments.

Bel, Decibel and Neper:

Decibel: Decibel (dB):

- Decibel is unit for expressing the ratio between two physical quantities like acoustic or electrical power or loudness of sounds.
- One decibel equals 10 times the common logarithm of the power ratio.

$$\text{Decibel (dB)} = 10 \log (P_2/P_1)$$

Where, $\frac{P_2}{P_1}$ represents power ratio.

Bel(B):

- Bel is a unit used for measuring sound intensity equal to 10 decibels.
- One Bel equals logarithm of the power ratio.

$$\text{Bel (B)} = \log (P_2/P_1)$$

Where, $\frac{P_2}{P_1}$ represents power ratio.

Neper:


- Neper is unit for expressing the ratio between two physical quantities like acoustic or electrical power or loudness of sounds.
- Neper is natural logarithm of the power ratio.

$$\text{Neper} = \ln (P_2/P_1)$$

Where, $\frac{P_2}{P_1}$ represents power ratio.

- 1Neper = 8.68dB.

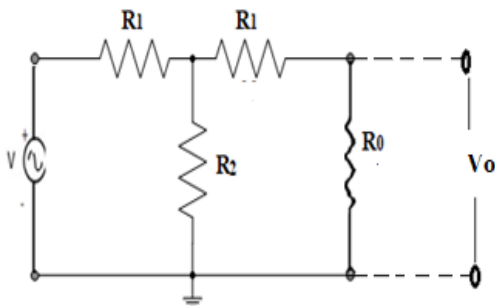Symmetric T attenuator: The symmetrical T-type attenuator is as shown below




$$R_1 = R_0 * (N-1) / (N+1)$$

$$R_2 = R_0 * 2N / (N^2 - 1)$$

Where, N is attenuation factor

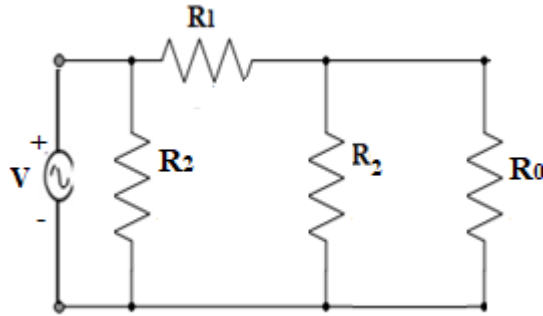Symmetric π attenuator: The symmetrical T-type attenuator is as shown below



$$R_1 = R_0 * (N+1) / (N-1)$$

$$R_2 = R_0 * (N^2 - 1) / 2N$$

Where, N is attenuation factor

Problems:

1. Design a T-type pad to give 25dB attenuation and to have characteristic impedance of 600 ohms.

Solution: Given, attenuation $D = 25\text{dB}$, $R_0 = 600\text{ohms}$

$$D = 20 \log N$$

$$\log N = D/20 = 25/20$$

$$N = \text{antilog}(25/20) = 10^{(25/20)}$$

$$N = 17.78$$

$$\text{w.k.t. } R_1 = [R_0 * (N-1)] / (N+1)$$


$$R_2 = [R_0 * 2N] / (N^2 - 1)$$

$$R_1 = [600 * (17.78 - 1)] / (17.78 + 1)$$

$$R_2 = [600 * 2 * 17.78] / (17.78^2 - 1)$$

$$R_1 = 536.10\Omega$$

$$R_2 = 6.770\Omega$$

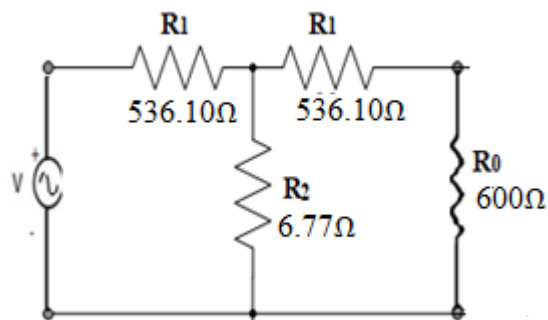

2. Design a π -type symmetrical attenuator to be inserted between 600Ω for an attenuation of 10dB.

Solution: Given, attenuation $D = 10\text{dB}$, $R_0 = 600\text{ohms}$

$$D = 20\log N$$

$$\log N = D/20 = 10/20$$

$$N = \text{antilog} (10/20) = 10^{(10/20)}$$

$$N = 3.162$$

$$\text{w.k.t. } R_2 = [R_0 * (N+1)] / (N-1)$$


$$R_1 = (N^2 - 1) / [R_0 * 2N]$$

$$R_2 = [600 * (3.162 + 1)] / (3.162 - 1)$$

$$R_1 = (3.162^2 - 1) / [600 * 2 * 3.162]$$

$$R_2 = 1155.04 \Omega$$

$$R_1 = 853.72 \Omega$$

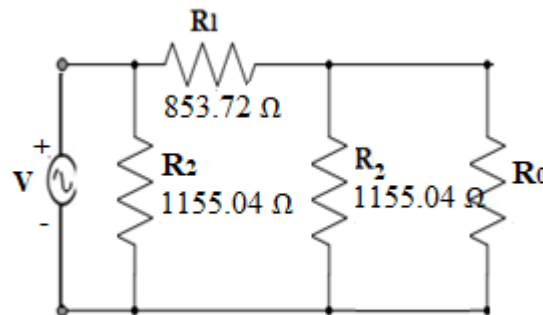

Activity:

1. An item in telecom system has an input resistance of 600Ω and correctly terminated. When an input voltage of 1.5 V is applied a current of 15mA flows in the load. Calculate the loss or gain of the system.
2. Design a T-type pad to give 10dB attenuation and to have characteristic impedance of 600 ohms.